

Name: Mofazzal Hosssain

Student Number: R00225120

Class Group: COMP1D-X

Lab 5 – De Morgan's Theorem and Basic Circuits


1. Prove the following theorems of De Morgan by completing the following tables.
Verify this theorem in Logisim using appropriate circuits:

(i) $\overline{A + B} = \overline{A} \cdot \overline{B}$

(ii) $\overline{A \cdot B} = \overline{A} + \overline{B}$


A	B	A+B	\overline{A}	\overline{B}	$\overline{A+B}$	$\overline{A} \cdot \overline{B}$
0	0	0	1	1	1	1
0	1	1	1	0	0	0
1	0	1	0	1	0	0
1	1	1	0	0	0	0

Circuits:

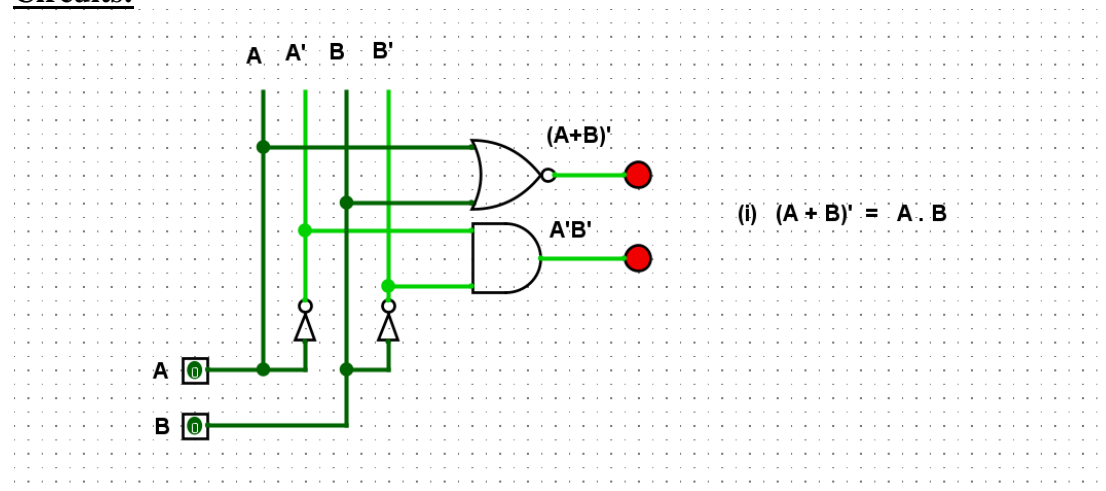

A	B	\overline{A}	\overline{B}	A.B	$\overline{A.B}$	$\overline{A} + \overline{B}$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0

Circuits:

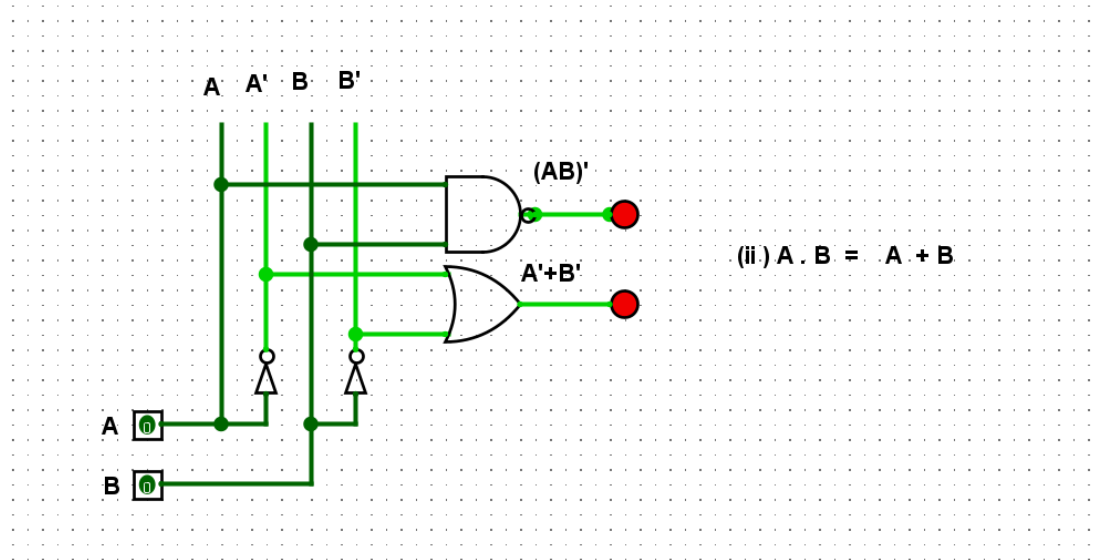


2. Draw circuits for the Boolean expressions outlined below. Complete the truth tables for these expressions and verify the truth tables using your circuits,

i. $x \cdot \overline{y \cdot z} + \overline{x}$

ii. $\overline{x}y + xz$

iii. $x + \overline{x} \cdot \overline{z}$

x	y	z	x'	y'	z'	xz	(yz)'	x'y	x'z'	x*(yz)'	$x \cdot \overline{y \cdot z} + \overline{x}$	$\overline{x}y + xz$	$x + \overline{x} \cdot \overline{z}$
0	0	0	1	1	1	0	1	0	1	0	1	0	1
0	0	1	1	1	0	0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	1	1	1	0	1	1	1
0	1	1	1	0	0	0	0	1	0	0	1	1	0
1	0	0	0	1	1	0	1	0	0	1	1	0	1
1	0	1	0	1	0	1	1	0	0	1	1	1	1
1	1	0	0	0	1	0	1	0	0	1	1	0	1
1	1	1	0	0	0	1	0	0	0	0	0	1	1

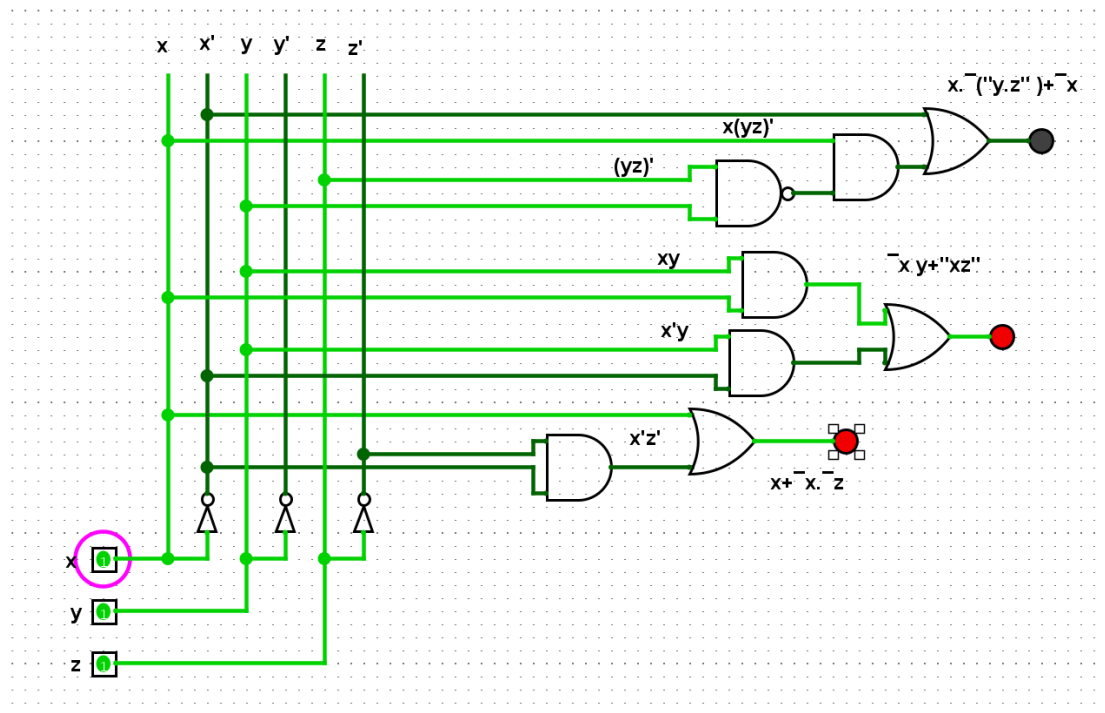

3. Using the Sum of Products technique, design a circuit which implements the following truth table. The inputs are A, B, and C. The output is X

Truth Table:

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Circuit:

$$X = (ABC)' + ABC' + AB'C + A'BC$$

