

Name: Mofazzal Hossain

Student Number: R00225120

Class Group: COMP1D-X

Lab 8 – K-Maps

Q1.

- Before simplifying, what is the Boolean expression for the truth table outlined below?
- Simplify using K-maps and design a circuit for the simplified expression. Draw the K-map below.
- Verify its operation using the simulator and paste a snapshot of your circuit below.

Truth Table:

| X | Y | Z | Output |
|---|---|---|--------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


$$\text{Output} = X'Y'Z' + XYZ' + X'YZ + XY'Z + XYZ$$

K-Map:

| XY \ Z | | Z | |
|--------|---|---|---|
| | | 0 | 1 |
| 00 | 1 | 1 | |
| 01 | 0 | 1 | |
| 11 | 0 | 1 | |
| 10 | 0 | 1 | |

$$\text{Output} = X'Y' + Z$$

Circuit

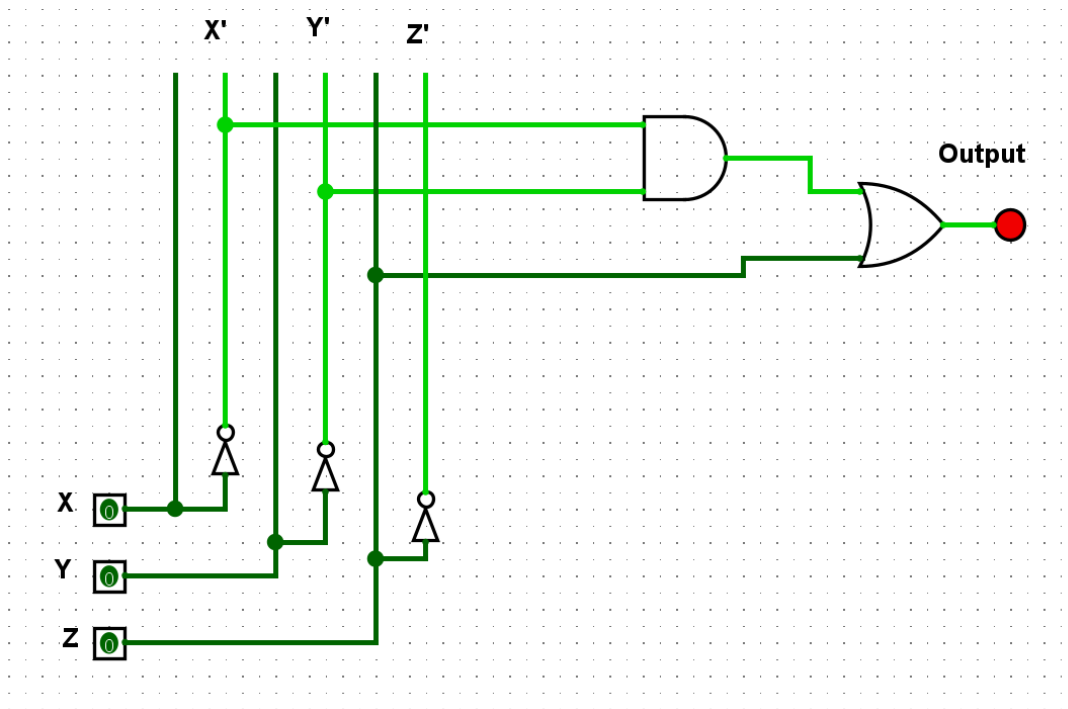

Q2.

- i) Design and simplify, using K-maps, a circuit for the following truth table. Draw the K-map below.
- ii) Verify its operation using the simulator and paste a snapshot of your circuit below.

Truth Table:


| A | B | C | D | Output |
|---|---|---|---|--------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | X |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | X |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

K-Map:

| AB \ CD | 00 | | 01 | | 11 | | 10 | |
|---------|----|----|----|----|----|----|----|----|
| | 00 | 01 | 11 | 10 | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 01 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 11 | 1 | X | 1 | 1 | 1 | 1 | 1 | 1 |
| 10 | x | 1 | 0 | 0 | 0 | 0 | 0 | 0 |

Output: $C'D' + B'C' + AB + BCD$

Circuit

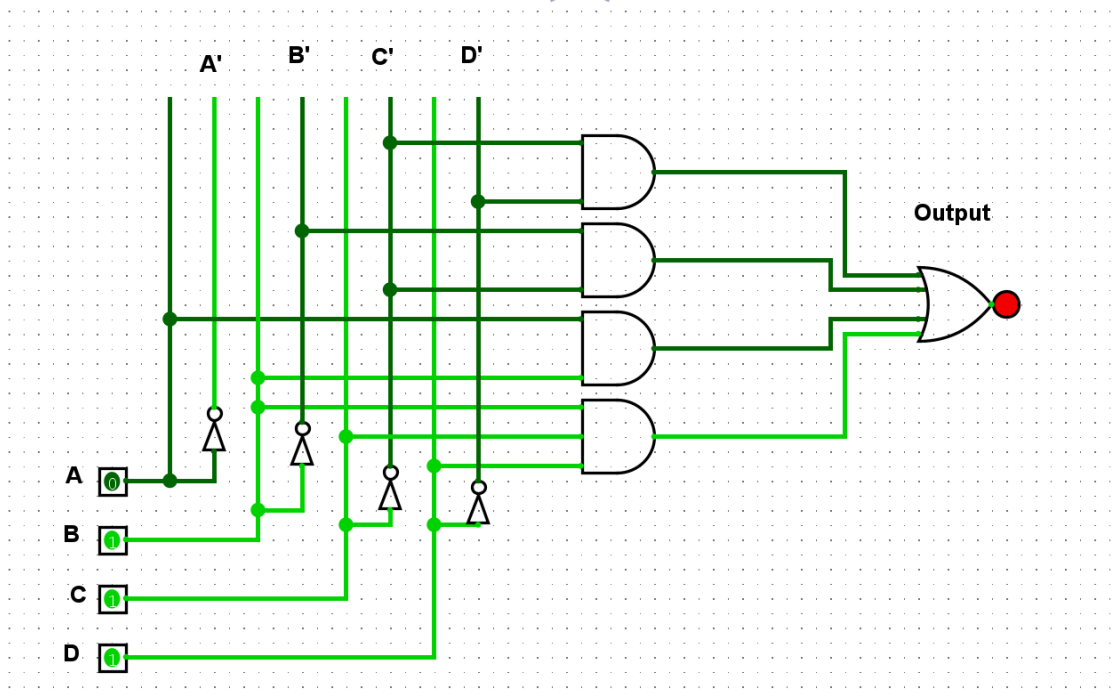

Q3.

- i) Design and simplify, using K-maps, a circuit for the following truth table. Draw the K-map below.
- ii) Verify its operation using the simulator and paste a snapshot of your circuit below.

Truth Table:

| X | Y | Z | Output |
|---|---|---|--------|
| 0 | 0 | 0 | X |
| 0 | 0 | 1 | X |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | X |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

K-Map:

| | | Z | |
|----|----|---|---|
| | | 0 | 1 |
| XY | 00 | X | X |
| | 01 | 1 | X |
| | 11 | 0 | 1 |
| | 10 | 1 | 0 |

| | | Z | |
|----|----|---|---|
| | | 0 | 1 |
| XY | 00 | X | X |
| | 01 | 1 | X |
| | 11 | 0 | 1 |
| | 10 | 1 | 0 |

Output: $X' + YZ + Y'Z'$

Circuit

