

Name: Mofazzal Hossain

Student Number: R00225120

Class Group: COMP1D-X

Lab 6 – Adders

1. Complete the following truth table for a binary half adder:


Truth Table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

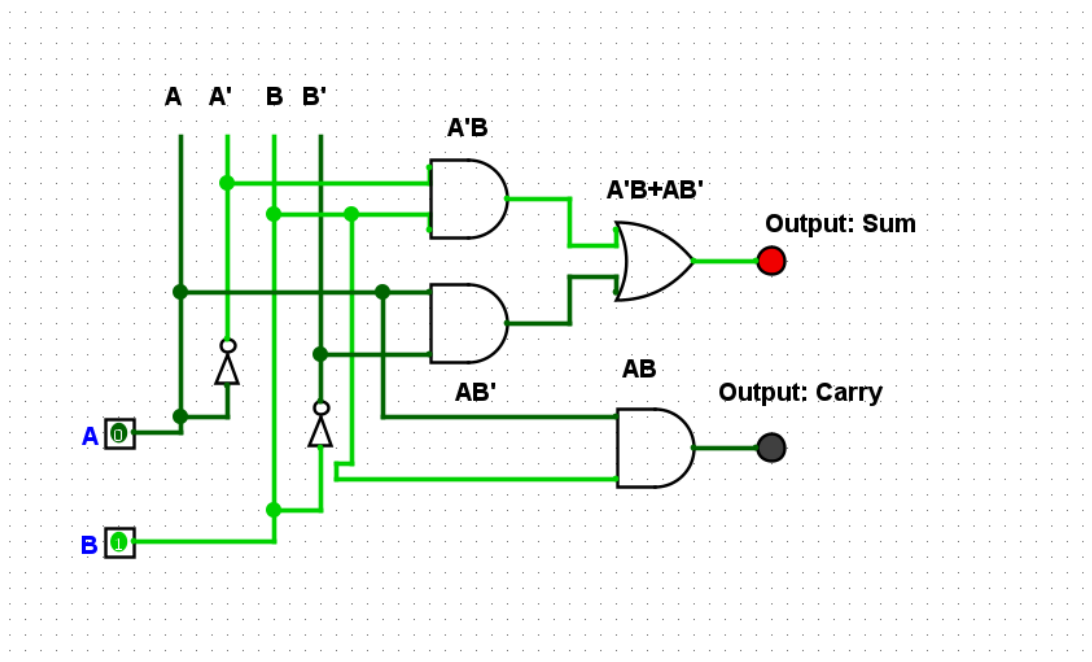
2. Using the truth table above, design a half adder circuit which adds two bits.

Circuit:

$$S = A' B + A B' \quad \text{or} \quad S = A \oplus B$$
$$C = AB$$



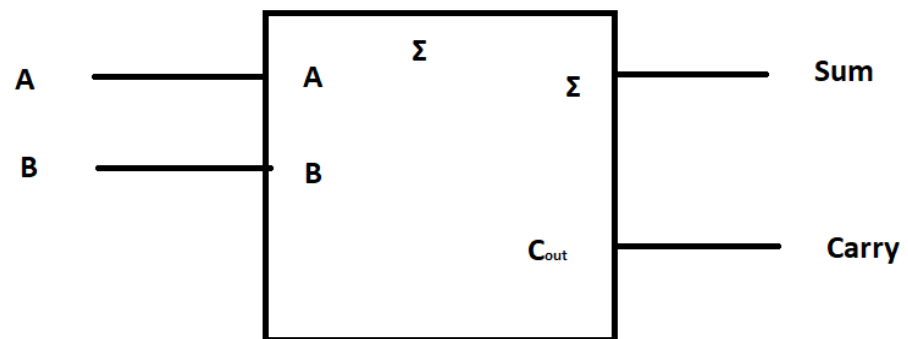
3. Draw the black box representation of a half adder.



4. Complete the following truth table for a full adder:


A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

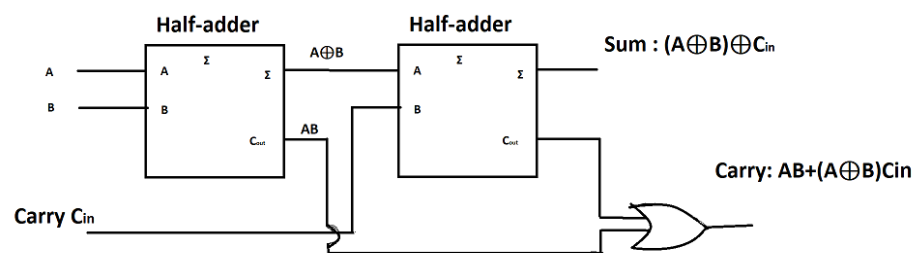5. Using the black box representation of a half adder (from Q.3), design a full adder which is capable of adding two bits and a carry-in bit.



6. Implement the full adder design in Logisim using XOR, AND and OR gates.


Circuit:

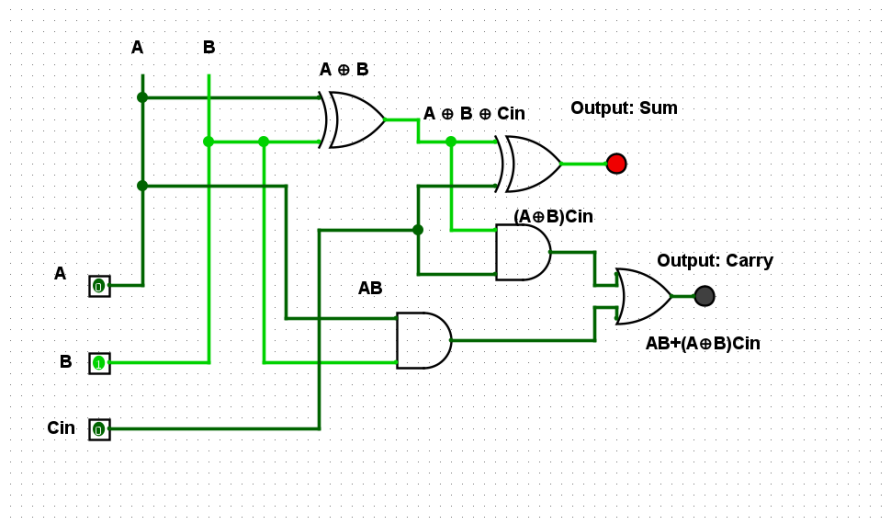

7. Using the partial circuit given on Canvas, ripple-burst.circ, complete the ripple carry adder which is capable of adding two 4-bit numbers. Test your circuit by adding the following 4-bit numbers (include a screenshot for each sum):

- a. $0011 + 0111 = 1010$
- b. $0101 + 0001 = 0110$
- c. $0011 + 0010 = 0101$
- d. $1000 + 0011 = 1011$
- e. $1010 + 0011 = 1101$
- f. $1101 + 1000 = 1010$ 1 # (Carry output 1)

Circuit:

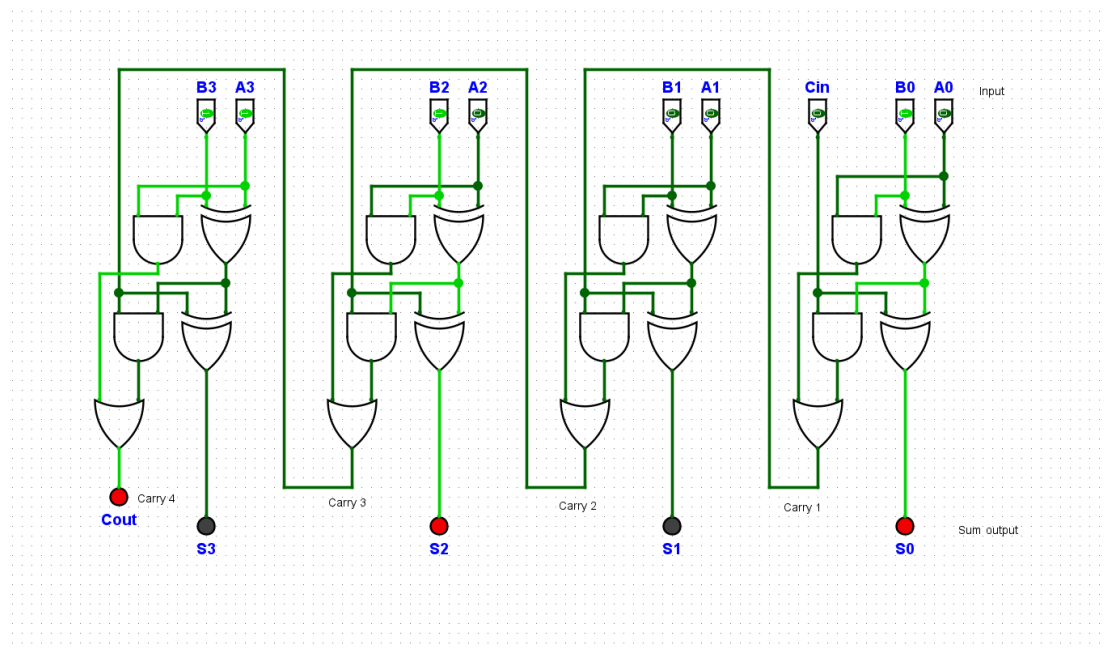

8. Using a black box design (i.e. use black box full adder blocks), draw the 4-bit ripple carry adder below:

